exercise: throughput/latency (1)

```
      cycle # 0 1 2 3 4 5 6 7 8

      0x100: add %r8, %r9
      F D E M W

      0x108: mov 0x1234(%r10), %r11
      F D E M W

      0x110: ...
      ...
```

suppose cycle time is 500 ps

exercise: latency of one instruction?

A. 100 ps B. 500 ps C. 2000 ps D. 2500 ps E. something else

exercise: throughput/latency (1)

```
      cycle # 0 1 2 3 4 5 6 7 8

      0x100: add %r8, %r9
      F D E M W

      0x108: mov 0x1234(%r10), %r11
      F D E M W

      0x110: ...
      ...
```

suppose cycle time is 500 ps

```
exercise: latency of one instruction?
```

A. 100 ps B. 500 ps C. 2000 ps D. 2500 ps E. something else

exercise: throughput overall?

A. 1 instr/100 ps B. 1 instr/500 ps C. 1 instr/2000ps D. 1 instr/2500 ps

E. something else


exercise: throughput/latency (2)


```
cycle #
0x100: add %r8, %r9
0x108: mov 0x1234(%r10), %r11
0x110: ...
                             cycle # 0 1 2 3 4 5 6 7 8
                                     F1 F2 D1 D2 E1 E2 M1 M2 W1 W
0x100: add %r8, %r9
0x108: mov 0x1234(%r10), %r11
                                       F1 F2 D1 D2 E1 E2 M1 M2 W
0x110: ...
```


double number of pipeline stages (to 10) + decrease cycle time from 500 ps to 250 ps — throughput?


A. 1 instr/100 ps B. 1 instr/250 ps C. 1 instr/1000ps D. 1 instr/5000 ps


E. something else

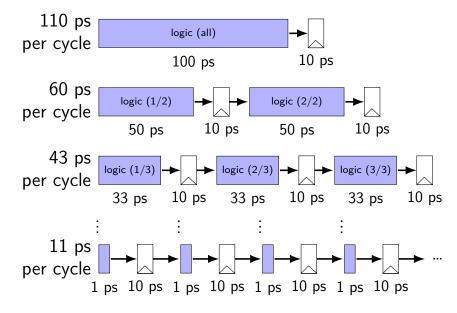


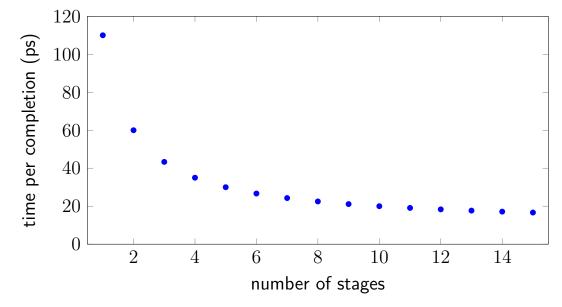

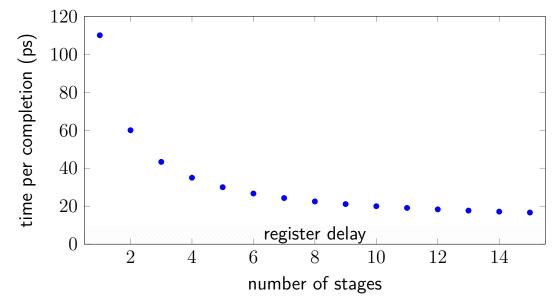

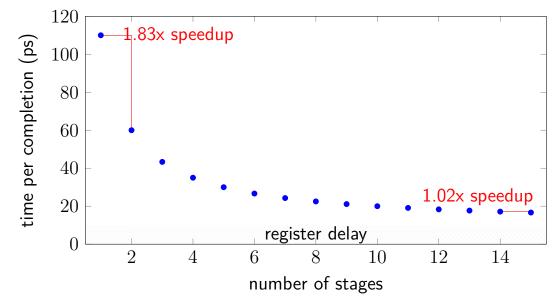

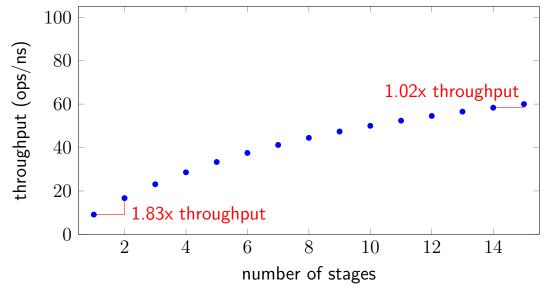


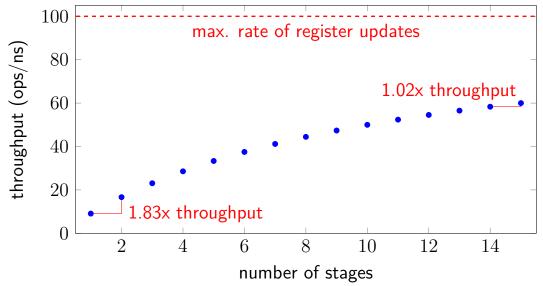

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?


Probably not...

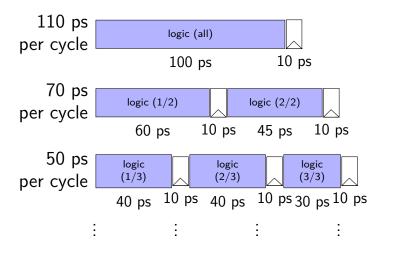

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?


Probably not...

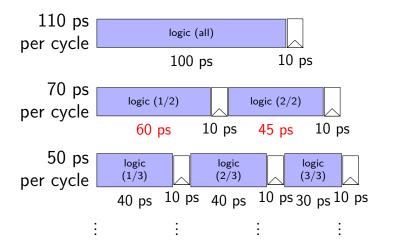

diminishing returns: uneven split

Can we split up some logic (e.g. adder) arbitrarily?

Probably not...

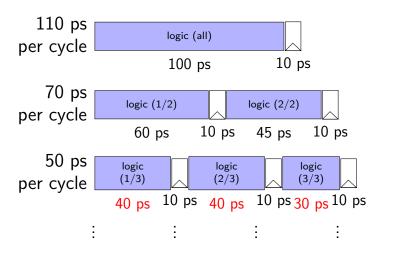

addq processor: data hazard

```
// initially %r8 = 800,
// %r9 = 900, etc.
addq %r8, %r9
addq %r9, %r8
addq ...
addq ...
```

	fetch	fetc	:h/decode	decode/execute		execute	execute/memory		memory/writeback	
cycle	PC	rA	rB	R[rB	R[rB]	rB	sum	rB	sum	rB
0	0x0		•						•	
1	0x2	8	9							
2		9	8	800	900	9				
3			•	900	800	8	1700	9]	
4					-		1700	8	1700	9
5									1700	8

addq processor: data hazard

```
// initially %r8 = 800,
// %r9 = 900, etc.
addq %r8, %r9
addq %r9, %r8
addq ...
addq ...
```

	fetch	fetc	:h/decode	decode/execute			execute	execute/memory		memory/writeback	
cycle	PC	rA	rB	R[rB	R[rB]	rB	sum	rB	sum	rB	
0	0x0		•			•			•		
1	0x2	8	9	7							
2		9	8 _	800	900	9					
3				900	800	8	1700	9]		
4				ld be		_	1700	8	1700	9	
5			1700	8							

data hazard

```
addq %r8, %r9 // (1)
addq %r9, %r8 // (2)
```

step#	pipeline implementation	ISA specification
1	read r8, r9 for (1)	read r8, r9 for (1)
2	read r9, r8 for (2)	write r9 for (1)
3	write r9 for (1)	read r9, r8 for (2)
4	write r8 for (2)	write r8 ror (2)

pipeline reads older value...

instead of value ISA says was just written

data hazard compiler solution


```
addq %r8, %r9
nop
nop
addq %r9, %r8
one solution: change the ISA
     all addqs take effect three instructions later
     (assuming can read register value while it is being written back)
make it compiler's job
problem: recompile everytime processor changes?
```

data hazard hardware solution

```
addq %r8, %r9
// hardware inserts: nop
// hardware inserts: nop
addq %r9, %r8
how about hardware add nops?
called stalling
extra logic:
    sometimes don't change PC
    sometimes put do-nothing values in pipeline registers
```

stalling/nop pipeline diagram (1)
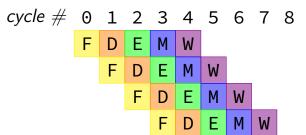
```
add %r8, %r9
(nop)
(nop)
addg %r9, %r8
```




stalling/nop pipeline diagram (1)


```
cycle # 0 1 2 3 4 5 6 7 8
add %r8, %r9
(nop)
(nop)
addg %r9, %r8
          assumption:
          if writing register value
          register file will return that value for reads
          not actually way register file worked in single-cycle CPU
```

(e.g. can read old %r9 while writing new %r9)

stalling/nop pipeline diagram (2)

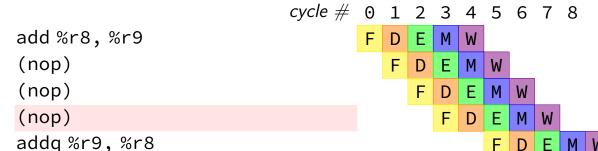

stalling/nop pipeline diagram (2)

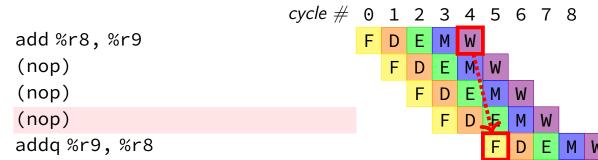


if we didn't modify the register file, we'd need an extra cycle

opportunity


```
// initially %r8 = 800,
// %r9 = 900, etc.
0x0: addq %r8, %r9
0x2: addq %r9, %r8
...
```

	fetch	fetc	h/decode	de	decode/execute			execute/memory		memory/writeback	
cycle	PC	rA	rB	R[rB	R[rB]	rB		sum	rB	sum	rB
0	0×0		•	•	•			•	•	•	
1	0x2	8	9								
2		9	8	800	900	9	_		_		
3			•	900	800	8		1700	9		
4		should be 1700 8									9
5											8

exploiting the opportunity

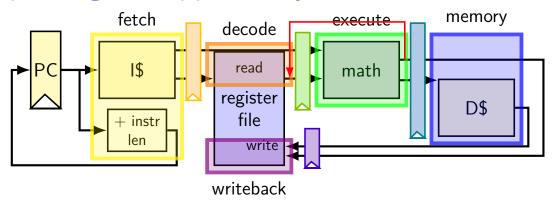

exploiting the opportunity

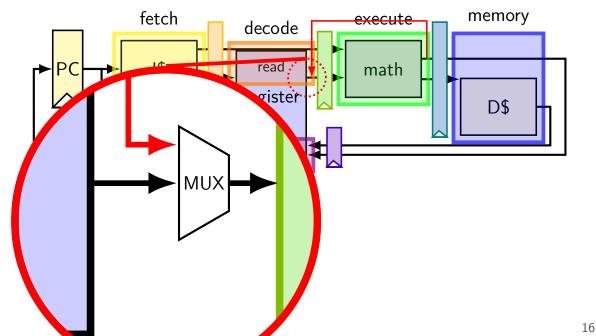


opportunity 2

```
// initially %r8 = 800,
// %r9 = 900, etc.
0x0: addq %r8, %r9
0x2: nop
0x3: addq %r9, %r8
```

	fetch	fetch	/decode	decode/execute		execute/memory		memory/writeback		
cycle	PC	rA	rB	R[rB	R[rB]	rB	sum	rB	sum	rB
0	0x0		•	•	•	•	•		•	•
1	0x2	8	9							
2	0x3			800	900	9				
3		9	8				1700	9		_
4				900	800	8			1700	9
5		1700 9								
6		should be 1700								9

exploiting the opportunity

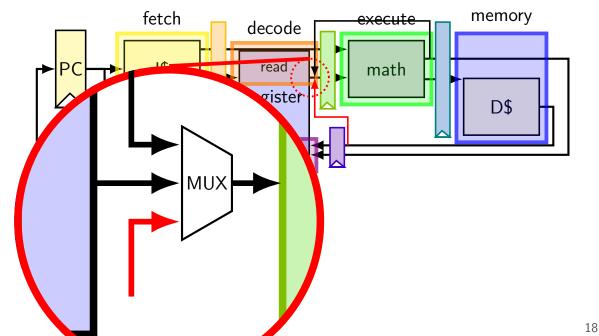

exercise: forwarding paths

 cycle #
 0
 1
 2
 3
 4
 5
 6
 7
 8

 addq %r8, %r9
 F
 D
 E
 M
 W
 W
 W
 W

in subq, %r8 is _____ addq.

in xorq, %r9 is _____ addq.


in andq, %r9 is _____ addq.

in andq, %r9 is _____ xorq.

A: not forwarded from

B-D: forwarded to decode from $\{\mbox{execute},\mbox{memory},\mbox{writeback}\}$ stage of


unsolved problem

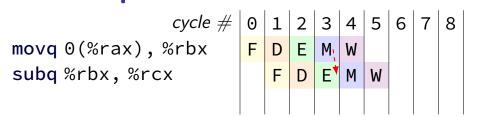

combine stalling and forwarding to resolve hazard

assumption in diagram: hazard detected in subq's decode stage (since easier than detecting it in fetch stage)


unsolved problem

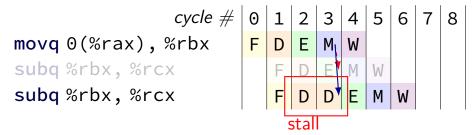


combine stalling and forwarding to resolve hazard

assumption in diagram: hazard detected in subq's decode stage (since easier than detecting it in fetch stage)

solveable problem

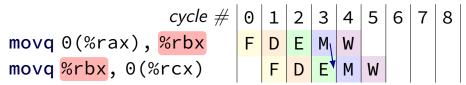


why can't we...

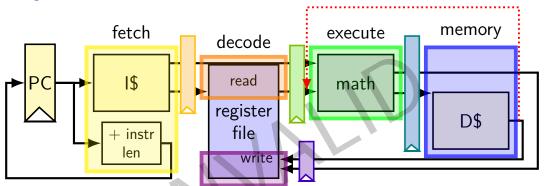

clock cycle needs to be long enough
to go through data cache AND
to go through math circuits!
(which we were trying to avoid by putting them in separate stages)

why can't we...

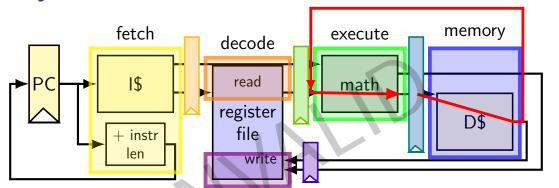

clock cycle needs to be long enough
to go through data cache AND
to go through math circuits!
(which we were trying to avoid by putting them in separate stages)

hazards versus dependencies

dependency — X needs result of instruction Y?

has potential for being messed up by pipeline
(since part of X may run before Y finishes)

hazard — will it not work in some pipeline?

before extra work is done to "resolve" hazards
multiple kinds: so far, data hazards

ex.: dependencies and hazards (1)

```
addq %rax, %rbx
subq %rax, %rcx
movq $100, %rcx
addq %rcx, %r10
addq %rbx, %r10
```

where are dependencies? which are hazards in our pipeline? which are resolved with forwarding?

ex.: dependencies and hazards (1)

```
addq %rax, %rbx
subq %rax, %rcx
movq $100, %rcx
addq %rcx, %r10
addq %rbx, %r10
```

where are dependencies? which are hazards in our pipeline? which are resolved with forwarding?

ex.: dependencies and hazards (1)

```
addq %rax, %rbx

subq %rax, %rcx

movq $100, %rcx

addq %rcx %r10

addq %rbx, %r10
```

where are dependencies? which are hazards in our pipeline? which are resolved with forwarding?

ex.: dependencies and hazards (1)

```
addq %rax, %rbx

subq %rax, %rcx

movq $100, %rcx

addq %rcx, %r10

addq %rbx, %r10
```

where are dependencies? which are hazards in our pipeline? which are resolved with forwarding?

pipeline with different hazards

```
example: 4-stage pipeline:
fetch/decode/execute+memory/writeback

// 4 stage // 5 stage
addq %rax, %r8 // // W
subq %rax, %r9 // W // M
xorq %rax, %r10 // EM // E
andq %r8, %r11 // D // D
```

pipeline with different hazards

```
example: 4-stage pipeline:
fetch/decode/execute+memory/writeback
              // 4 stage // 5 stage
addq %rax, %r8 // // W
subq %rax, %r9 // W // M
xorq %rax, %r10 // EM // E
andq %r8, %r11 // D // D
addg/andg is hazard with 5-stage pipeline
addq/andq is not a hazard with 4-stage pipeline
```

pipeline with different hazards

```
example: 4-stage pipeline:

fetch/decode/execute+memory/writeback

// 4 stage // 5 stage

addq %rax, %r8 // // W

subq %rax, %r9 // W // M

xorq %rax, %r10 // EM // E

andq %r8, %r11 // D // D
```

more hazards with more pipeline stages

split execute into two stages: F/D/E1/E2/M/W

result only available near end of second execute stage

where does forwarding, stalls occur?

cycle #	0	1	2	3	4	5	6	7	8	
(1) addq %rcx, %r9	F	D	E1	E2	М	W				
(2) addq %r9, %rbx										
(3) addq %rax, %r9										
(4) movq %r9, (%rbx)										
(5) movq %rcx, %r9										

cycle #	0	1	2	3	4	5	6	7	8	
addq %rcx, %r9	F	D	E1	E2	М	W				
addq %r9, %rbx										
addq %rax, %r9										
0. 0. (0. 1.)										
movq %r9, (%rbx)										
		:					:			

cycle #	0	1	2	3	4	5	6	7	8
addq %rcx, %r9	F	D	E1	E2	М	W			
addq %r9, %rbx		F	D	E1	E2	М	W		
addq %rax, %r9			F	D	E1	E2	М	W	
movq %r9, (%rbx)				F	D	E1	E2	M	W

cycle #	0	1	2	3	4	5	6	7	8	
addq %rcx, %r9	F	D	E1	E2	М	W				
addq %r9, %rbx		F	D	Ε1	E2	М	W			
addq %r9, %rbx		F	D	D	E1	E2	М	W		
addq %rax, %r9			F	D	E1	E2	М	W		
addq %rax, %r9			F	F	D	E1	E2	M	W	
movq %r9, (%rbx)				F	D	E1	E2	M	W	
movq %r9, (%rbx)					F	D	E1	E2	M	W

cycle #	0	1	2	3	4	5	6	7	8	
addq %rcx, %r9	F	D	E1	E2	М	W				
addq %r9, %rbx		F	D	Ε1	E2	М	W			
addq %r9, %rbx		F	D	D	E1	E2	М	W		
addq %rax, %r9			F	D	E1	E2	М	W		
addq %rax, %r9			F	F	D	E1	E2	M	W	
movq %r9, (%rbx)				F	D	E1	E2	M	W	
movq %r9, (%rbx)					F	D	E1	E2	M	W

movq %rcx, %r9

split execute into two stages: F/D/E1/E2/M/W cycle # 0 1 2 3 4 5 6 7 8 addq %rcx, %r9 D F1 F2 M addg %r9, %rbx F D E1 E2 M W addq %r9, %rbx D D E1 E2 M F D E1 E2 M W addg %rax, %r9 addq %rax, %r9 F D E1 E2 M movq %r9, (%rbx) F D E1 E2 M W movq %r9, (%rbx) F D E1 E2 M W

D F1 F2

control hazard

0x00: cmpq %r8, %r9

0x08: je 0xFFFF

0x10: addq %r10, %r11

	fetch	fetch-	decode ·	decode-	→execut	execute→writel	execu	te→writeback	
cycle	PC	rA	rB	R[rA]	R[rB]	result			
0	0×0								
1	0x8	8	9						
2	???			800	900				
3	???					less than			

control hazard

0x00: cmpq %r8, %r9

0x08: je 0xFFFF

0x10: addq %r10, %r11

	fetch	fetch $ ightarrow$	decode d	lecode-	→execute	execute→writel	execu	te→writeback	
cycle	PC	rA	rB	R[rA]	R[rB]	result			
0	0×0								
1	9×8	9	9						
2	???			800	900				
3	???					less than			

0xFFFF if R[8] = R[9]; 0x10 otherwise

```
cmpq %r8, %r9
       ine LABEL
                     // not taken
       xorq %r10, %r11
       movg %r11, 0(%r12)
                             cycle # 0 1 2 3 4 5 6 7 8
cmpq %r8, %r9
                                              М
ine LABEL
                                              Ε
                                                 М
                                           D
                                                   W
(do nothing)
                                                   М
(do nothing)
                                                    Е
                                                         W
xorg %r10, %r11
                                                   D
                                                         М
                                                            W
movg %r11, 0(%r12)
•••
```

```
cmpq %r8, %r9
       ine LABEL
                     // not taken
       xorq %r10, %r11
       movg %r11, 0(%r12)
                             cycle # 0 1 2 3 4 5 6 7 8
cmpq %r8, %r9
                          compare sets flags | E
ine LABEL
                                              Ε
                                           D
                                                 М
                                                    W
(do nothing)
                                                    М
(do nothing)
                                                    Е
                                                         W
xorg %r10, %r11
                                                    D
                                                         М
                                                            W
movg %r11, 0(%r12)
```

```
cmpq %r8, %r9
       ine LABEL // not taken
       xorq %r10, %r11
       movg %r11, 0(%r12)
                            cycle # 0 1 2 3 4 5 6 7 8
cmpq %r8, %r9
ine LABEL
           compute if jump goes to LABEL
(do nothing)
                                                 М
(do nothing)
                                                 Е
                                                      W
xorg %r10, %r11
                                                 D
                                                      М
                                                         W
movg %r11, 0(%r12)
```

```
cmpq %r8, %r9
       ine LABEL
                     // not taken
       xorq %r10, %r11
       movg %r11, 0(%r12)
                             cycle # 0 1 2 3 4 5 6 7 8
cmpq %r8, %r9
                                              М
ine LABEL
                                              Е
                                                    W
(do nothing)
                                                    М
(do nothing)
                                                    Ε
                                                         W
xorg %r10, %r11
                              use computed result | F
                                                         М
                                                            W
movq %r11, 0(%r12)
```

making guesses

```
cmpq %r8, %r9
jne LABEL
xorq %r10, %r11
movq %r11, 0(%r12)
...
```

```
LABEL: addq %r8, %r9 imul %r13, %r14
```

speculate (guess): jne won't go to LABEL

right: 2 cycles faster!; wrong: undo guess before too late

jXX: speculating right (1)

•••

```
cmpq %r8, %r9
       ine LABEL
       xorq %r10, %r11
       movg %r11, 0(%r12)
        . . .
LABEL: addg %r8, %r9
       imul %r13, %r14
        . . .
                               cycle # 0 1 2 3 4 5 6 7 8
cmpq %r8, %r9
                                             Е
                                                М
                                           D
jne LABEL
                                                Ε
xorq %r10, %r11
                                                D
                                                      М
movq %r11, 0(%r12)
                                                      Е
```

31

jXX: speculating wrong

```
0 1 2 3 4 5 6 7 8
               cycle #
cmpq %r8, %r9
ine LABEL
                               Е
                            D
                                    W
xorq %r10, %r11
                            F
                               D
(inserted nop)
movq %r11, 0(%r12)
                               F
(inserted nop)
                                    Е
                                         W
LABEL: addq %r8, %r9
                                         М
                                    D
imul %r13, %r14
```

jXX: speculating wrong

```
cycle # 0 1 2 3 4 5 6 7 8
cmpq %r8, %r9
ine LABEL
                          F
                             D
xorq %r10, %r11
                               D instruction "squashed"
(inserted nop)
movq %r11, 0(%r12)
                                  instruction "squashed"
(inserted nop)
                                     Е
                                          W
LABEL: addq %r8, %r9
                                          М
                                     D
imul %r13, %r14
```

"squashed" instructions

on misprediction need to undo partially executed instructions

mostly: remove from pipeline registers

more complicated pipelines: replace written values in cache/registers/etc.

performance

hypothetical instruction mix

kind	portion	cycles (predict not-taken)	cycles (stall)
taken jXX	3%	,	3
non-taken jXX	5%	1	3
others	92%	1*	1*

performance

hypothetical instruction mix

kind	portion	cycles (predict not-taken)	cycles (stall)
taken jXX	3%	,	3
non-taken jXX	5%	1	3
others	92%	1*	1*

backup slides